

V.A. MANDAL  
S.S. CLASS XI PHYSICS  
IX. 100

Current Electricity: - The study of electric charges in motion is called current electricity.

### Electric current

The flow of electric charges through a conductor constitutes electric current.

Quantitatively,

Electric current across an area

held perpendicular to the direction of flow of charge is defined as the amount of charge flowing across that area per unit time.

$$\text{For a steady flow of charge, } I = \frac{q}{t}$$

Current are not always steady and hence more generally we define the current as follows.

Let  $\Delta Q$  be the net charge flowing across a cross-section of a conductor during the time interval  $t$  and  $t + \Delta t$ . Then the current at a time 't' across the cross-section of the conductor is defined as

$$I(t) = \frac{\Delta Q}{\Delta t} \quad (\text{unit Coulomb})$$

S.I unit of current : Ampere

Current  $I = \frac{q}{t}$  having the unit

depends on velocity  $v$  &  $\Delta t$  (length of area)

$$= \frac{\text{Coulomb}(C)}{\text{Second}(s)} = \text{Ampere(A)}$$

## Definition of 1 Ampere.

If one coulomb of charge crosses an area in one second then the current through that area is one Ampere.

$$1 \text{ Ampere} = 1 \text{ Coulomb} / \text{second}$$

$$Ampere = \frac{\text{Coulomb}}{\text{Second}}$$

## Conventional Current and Electronic current.

The direction of motion of positive charges is taken as the direction of conventional current. Since electrons being negatively charged, so the direction of electric current or electronic current is opposite to that of the conventional current.

Q. Is electric current a scalar or a vector quantity? Give reason.

Electric current has both magnitude and direction but it is considered as a scalar quantity because it does not obey the laws of vector addition or subtraction.

## Ohm's law.

The law states that the current flowing through a conductor is directly proportional to the potential difference applied across its ends provided the temperature and other physical conditions remains unchanged.

$$(A) \propto (V) \propto I$$

Thus Potential difference  $\propto$  current.

or

$$V = RI$$

The proportionality constant  $R$  is called the resistance of the conductor.

Resistance: It is the property by virtue of which a conductor opposes the flow of charges through it. It is equal to the ratio of the potential difference applied across the conductor to the current flowing through it.

$$R = \frac{V}{I}$$

## SI unit of Resistance = Ohm (Ω).

i.e. SI unit of resistance =  $\frac{\text{Volt}}{\text{Ampere}}$  = Ohm.

## Definition of 1 ohm.

The resistance of a conductor is  $1\Omega$  if a current of 1 Ampere flows through it on applying a potential difference of 1 Volt across its ends.

$$\text{or } 1\Omega = \frac{1\text{V}}{1\text{A}}$$

## Factors affecting the resistance.

1. The resistance  $R$  of a conductor is directly proportional to the length ' $l$ '
2. The resistance  $R$  of a conductor is inversely proportional to the area ' $A$ '.

fional to its area of cross-section;

$$i.e. R \propto \frac{1}{A}$$

### 3. Nature of the material.

Combining the above factors we get

$$R \propto \frac{l}{A}$$

$$R = \frac{\rho l}{A}$$

where  $\rho$  is the constant of proportionality, called resistivity or specific resistance of the material of the conductor.

### Resistivity or Specific resistance

$$We know - that R = \frac{\rho l}{A}$$

if  $l = 1\text{m}$  and  $A = 1\text{m}^2$ , then if

$R = \rho l$ . Then  $\rho = \frac{R}{l}$

Thus the resistivity or specific resistance of a material may be defined as the resistance of a conductor, having unit length and unit area of cross-section.

### S.I units of resistivity

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{R A}{l}$$

S.I unit of  $\rho$  is  $\frac{\Omega \text{ m}^2}{\text{m}}$  (metre)

in SI units it is  $\frac{\Omega \text{ m}}{\text{m}}$  or  $\frac{\Omega}{\text{m}}$

### Current Density

(i) Current per unit area is called current density. It is denoted by  $j$ .

$$j = \frac{I}{A}$$

S.I unit of current density =  $\text{A/m}^2$ .

### Conductance

It is defined as the reciprocal of the resistance. i.e.  $G = \frac{1}{R}$

$$G = \frac{1}{R}$$

The S.I unit of conductance is  $\frac{1}{\Omega} = \text{S}$

or mho ( $\text{S}^{-1}$ ) or Siemens (S)

### Conductivity

The reciprocal of the resistivity of a material is called Conductivity.

$$i.e. \text{Conductivity } \sigma = \frac{1}{\rho}$$

Conductivity is related to resistivity as

$$\sigma = \frac{1}{\rho}$$

Then S.I unit of conductivity is  $\frac{\text{A}}{\text{m}^2} = \frac{\text{A}}{\text{m}^2} = \text{S m}^{-1}$

## Ohm's law in vector form

If  $E$  is the magnitude of electric field in a conductor of length ' $l$ ', then the potential difference across its ends is

$$V = El \quad \text{--- (1)}$$

Also from Ohm's law

$$V = IR$$

$$El = I \frac{Rl}{A} \text{ from (1) :}$$

$$\therefore E = \frac{I R}{A} \text{ from (1) :}$$

$$\therefore E = jS \text{ where } j = I/A \text{ current density.}$$

As the direction of current density  $j$  is same as that of electric field  $E$ ,

$$\vec{E} = S \vec{j}$$

$$\text{or } \vec{j} = \frac{\vec{S}}{S}$$

$$\boxed{\vec{j} = \sigma \vec{E}} \quad \text{where } \sigma = \frac{1}{S} \text{ called conductivity.}$$

The above equation is the vector form of Ohm's law. It is equivalent to the scalar form  $V = RI$ .

## Classification of solids on the basis of resistivity

On the basis of their resistivity values, solids can be classified into three categories.

1. Conductors - Metals have low resistivities in the range  $10^{-8} \Omega m$  to  $10^{-6} \Omega m$ . These are also known as good conductors of electricity. They easily allow current to flow through them.

2. Insulators - These are the substances which have large resistivities, more than  $10^4 \Omega m$ . Insulators like glass and rubber have resistivities in the range  $10^{14}$  to  $10^{16} \Omega m$ .

3. Semiconductors - These are the substances having resistivities between those of conductors and insulators, between  $10^6 \Omega m$  to  $10^8 \Omega m$ . Germanium and silicon are typical semiconductors.

## Drift velocity and Relaxation time

In the absence of any electric field, the free electrons of a metal are in a state of continuous random motion. The average random velocity of free electrons is zero.

$$\vec{u} = \frac{\vec{u}_1 + \vec{u}_2 + \vec{u}_3 + \dots + \vec{u}_n}{n} = 0$$

$$\text{for } \frac{1}{n} \sum_{i=1}^n \vec{u}_i = 0 \text{ since all velocities are random}$$

Thus there is no net flow of charge in any given direction.

In the presence of an external electric field  $\vec{E}$ , each electron experiences a force  $F = q\vec{E}$  or  $= -e\vec{E}$  in the opposite direction of  $\vec{E}$ ; and undergoes an acceleration  $a$  is given by

$$\vec{a} = \frac{-e\vec{E}}{m}$$

$$\begin{cases} F = ma \\ a = F/m \end{cases}$$

where 'm' is the mass of an electron.  
 As the electrons accelerate, they frequently collide with the other electrons of the metal. Between two successive collisions, an electron gains a velocity component in a direction opposite to  $\vec{E}$ . However, the gain in velocity lasts for a short time and is lost in the next collision. After each collision each electron makes a fresh start. The average time interval between successive collisions of an electron is called relaxation time. It is given by.

$$\tau = t_1 + t_2 + \dots + t_N$$

During the relaxation time  $\tau$ , as electrons gains an average velocity given by.

$$\begin{aligned} \text{Average velocity } \vec{v}_d &= \vec{u}_0 + \vec{a} \tau \\ &= 0 + \vec{a} \tau \\ \vec{v}_d &= -\frac{e\vec{E}}{m} \tau \end{aligned}$$


The parameter  $\vec{v}_d$  is called drift velocity of electrons.

Drift velocity of electrons is defined as the average velocity gained by the free electrons of a conductor in the opposite direction of the externally applied electric field.

### Relation between electric current and drift velocity.

Consider a conductor of length 'l' and area of cross-section A applied to a potential difference 'V'. The electric field ' $E$ ' set up inside the conductor is given by

$$E = \frac{V}{l}$$

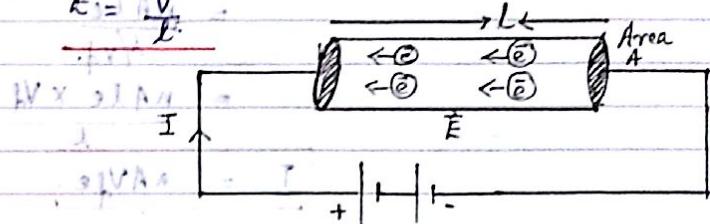

Under the influence of field  $\vec{E}$  the free electrons begin to drift in the opposite direction of  $\vec{E}$ .

Number of electrons per unit volume =  $n$ .

Charge of an electron =  $e$ .

Electron density 'n' =  $\frac{\text{Total number of electrons}}{\text{Volume of the conductor}}$

$$n = \frac{N}{AL} \quad \begin{matrix} \text{and } N \rightarrow \text{number} \\ \text{of electrons} \end{matrix}$$

Total charge 'q' =  $N \times \text{charge of an electron}$

$$= Nx e$$

$$\text{and this is } NAL \times e = iALe.$$

- All the electrons which enter the conductor at the right end will pass through the conductor at the

left end in line. - which initial initial  
 $t = \frac{\text{distance}}{\text{velocity}}$

Now it has a velocity  
 $v_d$  & voltage applied to one end.

$$\text{current} I = \frac{q}{t} = \frac{nAe}{t} \cdot v_d$$

$$= \frac{nAe^2}{t \cdot nvd}$$

$$= \frac{nAe^2}{l} \cdot v_d$$

$$\boxed{I = nAV_d e.}$$

This equation relates the current  $I$ , with the drift velocity  $v_d$ . Now all we have to do is to relate current density  $j = \frac{I}{A}$

$$\text{current density } j = \frac{I}{A}$$

$$j = \frac{nAv_d e}{A}$$

$$\boxed{j = nV_d e.}$$

leads to relation between  $j$  &  $I$

denoted it to  $nvd$

### Deduction of Ohm's law.

Consider a conductor of length  $l$  and area of cross-section  $A$  containing  $n$  free electrons per unit volume. Let the potential difference  $V$  be applied between its ends.

Electric field is set up inside the

conductor  $E = \frac{V}{l}$  - ①

If 'm' is the mass of an electron and 'T' is the relaxation time then drift velocity

$$v_d = \frac{eE}{m} T. - ②$$

$$\text{But } E = \frac{V}{l}$$

$$\therefore \text{the above eqn becomes. } v_d = \frac{e}{m} \frac{V}{l} \cdot T. - ③$$

$$\text{current } I = nAV_d e.$$

$$= nA \left( \frac{e}{m} \frac{V}{l} T \right) e \quad \text{from eqn (3)}$$

$$I = \frac{n^2 T A}{l} \cdot V$$

$$\boxed{\frac{V}{I} = \frac{ml}{n^2 TA}} \quad \text{At fixed temperature}$$

the quantities 'm', 'l', 'n', 'e' T and A all have constant values for a given conductor.

$\therefore \frac{V}{I} = \text{a constant called the resistance } R.$

This proves Ohm's law for a conductor and hence

$$\boxed{R = \frac{ml}{n^2 TA}}$$

Conductivity -  $\sigma = \frac{1}{R}$  (from ohm's law)

The resistance  $R$  of a conductor of length  $l$ , area of cross-section  $A$  and resistivity  $\rho$  is given by

$$\boxed{R = \frac{\rho l}{A}}$$

$$\text{But } R = \frac{ml}{n^2 TA}$$

where  $T$  is the relaxation time. Comparing the

From above two equations, we get:  $\frac{S.K}{A} = \frac{mK}{n e^2 T}$

$$S = \frac{m}{n e^2 T}$$

Obviously 'S' is independent of the dimensions of the conductor but depends on its two parameters.

i. Number of free electrons per unit volume or electron density of the conductor.

ii. The relaxation time 'T', the average time between two successive collisions of an electron.

### Mobility:

The mobility of a charge carrier is the drift velocity per unit electric field.

$$\mu = \frac{V_d}{E}$$

where  $V_d$  is the drift velocity and  $E$  is the electric field.

or  $V_d = \frac{e E T}{m}$  where  $V_d = e E T$ .

$$\therefore \mu = \frac{e T}{m}$$

where  $T$  is the relaxation time. Mobility is always positive.

$$8. I \text{ unit of mobility} = \frac{m/s}{V/m} = \frac{m \times m/s}{s \times V}$$

$$= \frac{m^2 s^{-1} V^{-1}}{V}$$

$$\text{Practical unit of mobility} = \text{cm}^2 \text{s}^{-1} \text{V}^{-1}$$

- CBSE Ques. What do you understand by the resistivity of a conductor? Discuss its temperature dependence for a conductor.
- metallic conductor
  - semiconductor
  - ionic conductor
  - electrolyte.

Ans: Resistivity of a material is the resistance of a conductor of that material, having unit length and unit area of cross-section.

If it is given by  $S = \frac{m}{n e^2 T}$

(i) In metallic conductor i.e. in metals - the number of free electrons is fixed. As the temperature increases the amplitude of vibration of the atoms increases. The collision of electrons with these atoms become more frequent. The relaxation time  $T$  decreases. Hence the resistivity of a metallic conductor increases with the increase of temperature.

(ii) In case of semiconductors, the relaxation time  $T$  does not change with temperature but the number density of free electrons increases exponentially with the increase in temperature. Consequently the conductivity increases or resistivity decreases exponentially with the increase in temperature.

(iii) Ionic conductors: - An ionic conductor has both positive and negative ions as the charge carriers. As the temperature increases, the electrostatic attraction between cations and anions decrease, the ions are more free to move and so the conductivity increases or resistivity decreases.

(iv) Electrolytes: As the temperature increases the interionic attractions decrease and also the viscous forces decrease, the ions move more freely. Hence conductivity or the resistivity decreases as the temperature of an electrolytic solution increases.

### Temperature coefficient of resistivity

The temperature coefficient of resistivity may be defined as the increase in resistivity per unit resistivity per degree rise in temperature.

$$\alpha = \frac{\delta - \delta_0}{\delta_0(T - T_0)}$$

$$\delta = \delta_0 + \alpha \delta_0 (T - T_0) \quad \text{--- (1)}$$

$$\text{where } \delta = \delta_0 [1 + \alpha (T - T_0)] \text{ this eqn (1)}$$

represents the resistivity at any temperature  $T$ , and  $\delta_0$  is the resistivity at a lowest temperature  $T_0$ .

As  $R = \delta \cdot \frac{l}{A}$  the dimensions and units of  $A$  are irrelevant.

hence  $R \propto \delta$  without loss of generality.

Hence eqn (1) can be written in terms of resistance as the initial resistance at  $t = R_0(1 + \alpha t)$  where  $R_0$  is the resistance at  $0^\circ\text{C}$ .

where  $R_0$  = the resistance at  $0^\circ\text{C}$ .

if  $R_0$  = the resistance at  $0^\circ\text{C}$  and let  $t$  be the rise in temperature =  $(T - T_0)$  then  $R = R_0(1 + \alpha t)$

8. I unit and dimension of  $\alpha$ :

We know that  $\alpha = \frac{\delta - \delta_0}{\delta_0(T - T_0)}$

$$8. I \text{ unit of } \alpha = \frac{\Omega \text{ m}}{\Omega \text{ m} \cdot {}^\circ\text{C}} = \frac{{}^\circ\text{C}^{-1}}{=}$$


$$\text{and dimension} = (\text{Temperature})^{-1} = \text{K}^{-1}$$

Distinguish between metals, semiconductors and alloys on the basis of their  $\alpha$  values.

For metals  $\alpha$  is positive, i.e. resistance of metals increases with the increase in temperature.

For semiconductors and insulators  $\alpha$  is negative, the resistance decreases with the increase in temperature.

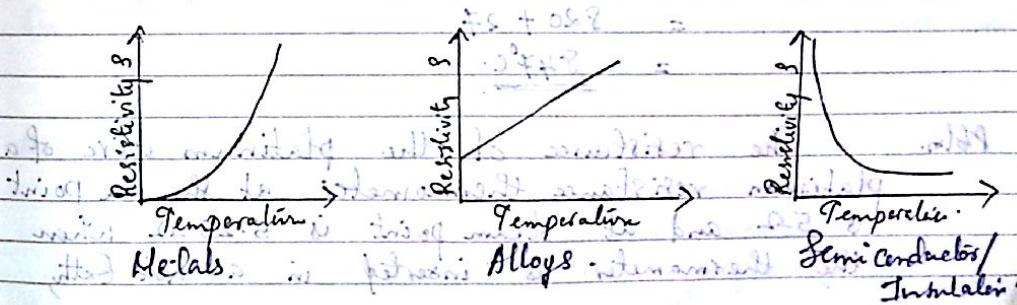For alloys like Pt constant, nichrome and manganin the temperature coefficient of resistance  $\alpha$  is very small, so they are used for making standard resistors.



**Ques:** An electric toaster uses nichrome for its heating element. When a negligibly small current passes through it, its resistance at room temperature is found to be  $75.3\ \Omega$ . When the toaster is connected to a  $230\text{ V}$  supply, the current settles after a few seconds to a steady value of  $2.68\text{ A}$ . What is the steady temperature of the nichrome element?  
 $\alpha$  of nichrome =  $1.70 \times 10^{-4}\text{ }^{\circ}\text{C}^{-1}$

$$R_0 = 75.3\ \Omega \text{ (at } 0^{\circ}\text{C})$$

$$R_t = \frac{230}{2.68} = 85.8\ \Omega$$

$$\therefore \alpha = 1.70 \times 10^{-4}\text{ }^{\circ}\text{C}^{-1}$$

Ans:  $R_t = R_0(1 + \alpha t)$  is a linear ref.  
 and  $t$  is constant for steady state condition.

$$R_t = R_0 + R_0 \alpha t$$

$$\therefore R_t - R_0 = R_0 \alpha t$$

$$t = \frac{R_t - R_0}{R_0 \alpha} = \frac{85.8 - 75.3}{75.3 \times 1.70 \times 10^{-4}}$$

$$\therefore t = \frac{85.8 - 75.3}{820 \times 10^{-4}} = 820^{\circ}\text{C}$$

$$T = T_0 + t = 820 + 70 = 890^{\circ}\text{C}$$

$$= 820 + 27$$

$$= 847^{\circ}\text{C}$$

**Ques:** The resistance of the platinum wire of a platinum resistance thermometer at the ice point is  $5\ \Omega$  and at steam point is  $5.23\ \Omega$  when the thermometer is inserted in a hot bath.

the resistance of the platinum wire is  $5.795\ \Omega$ . Calculate the temperature of the bath.

$$\text{Soln: } R_0 = 5\ \Omega \quad R_{100} = 5.23\ \Omega$$

$$R_t = 5.795\ \Omega$$

$$\text{As } R_t = R_0(1 + \alpha t)$$

$$R_t - R_0 = R_0 \alpha t \quad \dots \text{--- (1)}$$

$$\text{and } R_{100} - R_0 = R_0 \alpha \times 100 \quad \dots \text{--- (2)}$$

$$\begin{aligned} \text{(1)} &\Rightarrow \frac{R_t - R_0}{R_{100} - R_0} = \frac{R_0 \alpha t}{R_0 \alpha \times 100} \\ &\text{(2)} \end{aligned}$$

$$\frac{R_t - R_0}{R_{100} - R_0} = \frac{t}{100}$$

$$\therefore t = \frac{R_t - R_0}{R_{100} - R_0} \times 100$$

$$= \frac{5.795 - 5}{5.23 - 5} \times 100$$

$$= \frac{0.795}{0.23} \times 100$$

$$= 345.65^{\circ}\text{C}$$

**Ques:** Why alloys like constantan or manganin are used for making standard resistor?


**Ans:** This is because of the following reasons.

- These alloys have high value of resistivity
- They have very small temperature coefficient
- So, their resistance does not change appreciably


- (iii) even for several degrees rise of temperature.  
 (iii) They are least affected by atmospheric conditions like air moisture etc.

### Limitations of Ohm's law.

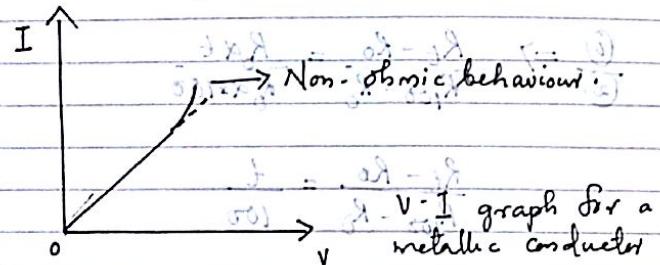
- (i) When a large current flows through a metallic conductor, it gets heated up and its resistance increases. The V-I graph becomes non-linear i.e. the conductor becomes non-ohmic at higher currents.



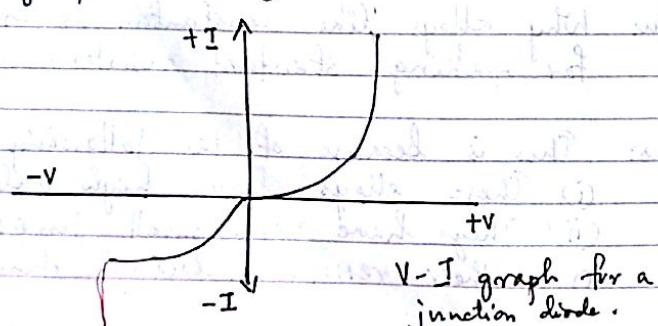- (ii) The relation between  $V$  and  $I$  depends on the sign of  $V$ . In other words, if  $I$  is the current for a certain  $V$ , then reversing the direction of  $V$  keeping its magnitude fixed, does not produce a current of the same magnitude as  $I$  in the opposite direction.  
 e.g.: V-I graph for a junction diode.



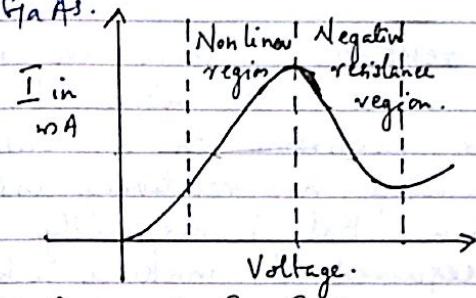- (iii) The relation between  $V$  and  $I$  is not unique i.e. there is more than one value of  $V$  for the same current. A material exhibiting such behaviour is GaAs.



### Resistivity of Various Materials.

On the basis of their resistivity values, solids can be classified into following three categories.

1. Conductors:- Metals have low resistivities in the range of  $10^{-8} \Omega\text{m}$  to  $10^{-6} \Omega\text{m}$ . These are known as good conductors of electricity.
2. Insulators:- These are the substances which have large resistivities more than  $10^4 \Omega\text{m}$ . Insulators like glass and rubber have resistivities in the range  $10^{14} \Omega\text{m}$  to  $10^{16} \Omega\text{m}$ .
3. Semiconductors:- These are the substances having resistivities between those of conductors and insulators i.e. between  $10^{-6} \Omega\text{m}$  to  $10^4 \Omega\text{m}$ . Germanium and silicon are typical semiconductors.

## Common Commercial resistors

The commercial resistors are of two types

1. Wire wound resistors:- These are made by winding the wires of an alloy like manganin, constantan or nichrome on an insulating base. These alloys are relatively insensitive to temperature. But inconveniently large length is required for making a high resistance.

2. Carbon resistors:- They are made from mixture of carbon black, clay and resin binders which are pressed and then mounted moulded into cylindrical rods by heating. The rods are enclosed in a ceramic or plastic jacket.

The carbon resistors are widely used in electronic circuits of radio receivers, amplifiers etc.

They have the following advantages.

\* They can be made with resistance values ranging from few ohms to several million ohms.

\* They are quite cheap and compact.

\* They are good enough for many purposes.

## Colour code for resistors

A colour code is used to indicate the resistance value of a carbon resistor and its percentage accuracy.

### Resistor colour codes

Colour	Number	Multiplier	Tolerance (%)
Black	0	$10^0 = 1$	
Brown	1	$10^1$	
Red	2	$10^2$	
Orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	
Blue	6	$10^6$	
Violet	7	$10^7$	
Gray	8	$10^8$	
White	9	$10^9$	
Gold			5
Silver			10
'No Colour'			20

The resistors have a set of co-axial coloured rings. The first two bands from the end indicate the first two significant figures of the resistance in Ohms. The third band indicates the decimal multiplier. The last band stands for tolerance or possible variation in percentage about the indicated values.


eg: 

$$\begin{aligned} \text{The resistance value is} \\ R &= (47 \times 10^{-2}) \pm 5\% \\ &= 470 \Omega \pm 5\% \end{aligned}$$

## Electrical Energy and Power.
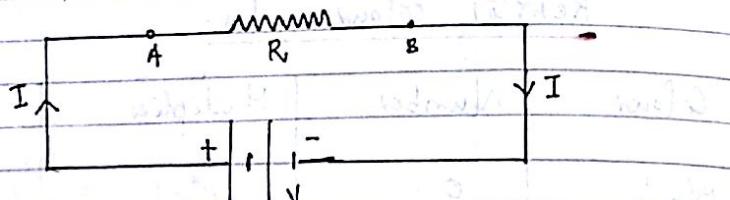
### Electrical Energy.

Consider a conductor AB of resistance R, shown in figure, in which a current I is flowing from A to B.



A source of emf maintains a potential difference  $V$  between its ends A and B and sends a steady current  $I$ .

Clearly  $V_A > V_B$

and the potential difference across AB is

$$V = V_{(AB)} - V_{(BA)} > 0. \quad \text{--- (1)}$$

The amount of charge that flows from A to B in time  $\Delta t$  is

$$\Delta Q = I \Delta t \quad \text{--- (2)}$$

Potential energy of the charge at A =  $\Delta Q V_{(A)}$

Potential energy of the charge at B =  $\Delta Q V_{(B)}$

Change in its potential energy

$$\begin{aligned} \Delta U_{\text{pot}} &= \text{final P.E.} - \text{Initial P.E.} \\ &= \Delta Q V_{(B)} - \Delta Q V_{(A)} \\ &= \Delta Q [V_{(B)} - V_{(A)}] \\ &= \Delta Q \times -V \\ &= -\Delta Q V \\ &= -I V \Delta t < 0 \quad \text{from (2)} \end{aligned}$$

If the charges move through the conductor without suffering collisions, their K.E. would change

By conservation of energy, the change in K.E. must be

$$\Delta K = -\Delta U_{\text{pot}}$$

$$\text{that is, } \Delta K = IV \Delta t > 0$$

Thus in case charges were moving freely through the conductor under the action of the electric field, their K.E. would increase as they move. But on the average, the electrons move with a steady drift velocity. This is because of the collisions of electrons with ions and atoms during the course of their motion.

The K.E. gained by the electrons is shared with the metal ions. These ions vibrate more vigorously and the conductor gets heated up. The amount of energy dissipated as heat in conductor is

time  $\Delta t$  is

$$\Delta W = IV \Delta t$$

According to Ohm's law  $V = IR$

$$\therefore \Delta W = \text{Heat} = I^2 R \Delta t$$

The above equation is known as Joule's law of heating.

According to this law, the heat produced in a resistor is

1. directly proportional to the square of current
2. directly proportional to the resistance R
3. directly proportional to the time  $t$  for which the current flows through the resistor.

### Electric Power.

The energy dissipated per unit time is the power

$$\therefore P = \frac{\Delta W}{\Delta t}$$

$$= \frac{IV\Delta t}{\Delta t}$$

$$P = IV \quad \text{--- (1)}$$

Using Ohm's law  $V = IR$ , we get.

$$P = I^2 R \quad \text{--- (2)}$$

$$P = \frac{V^2}{R} \quad \text{--- (3)}$$

as the power loss (Ohmic loss) in a conductor of resistance  $R$  carrying a current  $I$ .

### High Voltage power transmission.

Electric power is transmitted from power stations to homes and factories through transmission cables. These cables have resistance. Power is wasted in them as heat. If we want to minimise the power loss in the transmission cables connecting the power stations to homes and factories.

Let us consider a device  $R$  to which a power  $P$  is to be delivered via transmission cables having a resistance  $R_c$  to be dissipated by it finally. If  $V$  is the voltage across  $R$  and  $I$  current through it. Then

$$P = VI \quad \text{--- (1)}$$

The power wasted in transmission cables is

$$P_c = I^2 R_c$$

$$= \frac{P^2}{V^2} R_c \quad \text{from equ (1).}$$

Thus power wasted in the transmission cables is inversely proportional to the square of voltage. Hence to minimise the power loss, electric power is transmitted to distant places at high voltages and low currents. These voltages are stepped down by transformers before supplying to homes and factories.

### Combination of Resistors.


#### Resistance in Series.

Consider three resistances  $R_1$ ,  $R_2$  and  $R_3$  connected in series. When a potential difference  $V$  is applied across the combination, the same current  $I$  flows through each resistance.

By Ohm's law,

the potential drops across the three resistances are

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3.$$

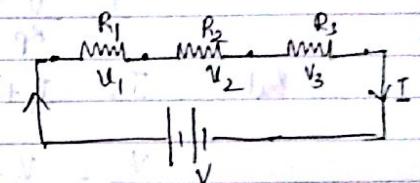

If  $R_s$  is the equivalent resistance of the series combination, then we must have

$$V = IR_s$$

$$\text{But } V = V_1 + V_2 + V_3.$$

$$IR_s = IR_1 + IR_2 + IR_3$$

$$R_s = R_1 + R_2 + R_3$$

Thus when a number of resistances are connected in series their equivalent resistance is equal to the sum of the individual resistances.

## 2. Resistances in parallel.

Consider three resistances  $R_1$ ,  $R_2$  and  $R_3$  connected in parallel between points A & B.

Let  $V$  be the potential difference applied across the combination.

Let  $I$ ,  $I_1$  and  $I_3$  be the currents through the resistances  $R_1$ ,  $R_2$  and  $R_3$  respectively. Then

$$\text{the current } I = I_1 + I_2 + I_3$$

Since all the resistances have been connected between the same two points A and B

∴ potential drop  $V$  is same across each of them.

By Ohm's law, the currents through the individual resistances will be:

$$I_1 = \frac{V}{R_1} \quad \text{and} \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3}$$

If  $R_p$  is the equivalent resistance of the parallel combination, then we must have

$$I = \frac{V}{R_p}$$

$$\text{But } I = I_1 + I_2 + I_3$$

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Thus when a number of resistances are connected in parallel, the reciprocal of the equivalent resistance of the parallel combination is equal to the sum of the reciprocals of the individual resistances.

## Cells, emf and Internal Resistance.

A simple device to maintain a steady current in an electric circuit is the electrolytic cell. A cell has two electrodes called (P) positive and (N) negative. They are immersed in an electrolytic solution. Dipped in the solution, the electrodes exchange charges with the electrolyte.


The positive electrode has a potential  $V_+$  between itself and the electrolyte solution. Similarly negative electrode develops a negative potential  $-V_-$  relative to the electrolyte.

When there is no current the electrolyte has the same potential throughout. So the potential difference between P and N is

$$V_+ - (-V_-) = V_+ + V_-$$

This difference is called the electromotive force (emf) of the cell and is denoted by  $E$ .

$$\text{Thus } E = V_+ + V_- > 0$$

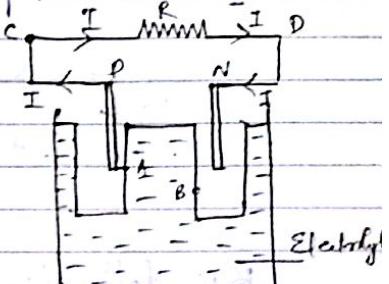

Internal resistance ( $\Omega$ ): The resistance offered by the electrolyte of a cell to the flow of current between its electrodes is called internal resistance of the cell. The internal resistance of a cell depends on the following factors:


1. Nature of the electrolyte.
2. Concentration of the electrolyte (directly).
3. distance between the two electrodes (directly).
4. Area of the electrodes (inversely).
5. Temperature of the electrolyte (inversely).

## Terminal Potential difference (V).

The potential drop across the terminals of a cell when a current is being drawn from it is called its terminal potential difference.
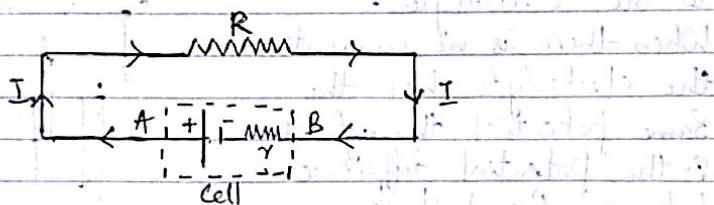
### Relation between $\epsilon$ , $V$ and $r$ .

Consider a cell of emf  $\epsilon$  and internal resistance ' $r$ ' connected to an external resistance  $R$ .



By definition of emf.

$\epsilon$  = Work done in carrying a unit charge from A to B against external resistance  $R$   
+ Work done in carrying a unit charge from B to A against internal resistance  $r$

$$\epsilon = V + V' \quad \text{--- (1)}$$

$$\epsilon = IR + Ir \quad \text{--- (2)}$$

$$\epsilon = I(R+r) \quad \text{--- (3)}$$

∴ Current in the circuit is distributed parallelly

$$I = \frac{\epsilon}{R+r}$$

Terminal P.d. of the cell is given by

$$V = \frac{\epsilon}{R+r} \cdot R_f = \frac{\epsilon R_f}{R+r} \quad \text{--- (2)}$$

Form (1)

Terminal P.d.

$$V = \epsilon - V'$$

$$V = \epsilon - Ir$$

$$r = \frac{\epsilon - V}{I}$$

$$= \frac{\epsilon - V}{V/R}$$


$$(V - V')R = (\frac{\epsilon - V}{V})R$$

∴ The internal resistance

$$r = \left( \frac{\epsilon - V}{V} \right) R$$

Ques. A network of resistors is connected to a 16V battery with internal resistance  $1\Omega$  as shown in figure.

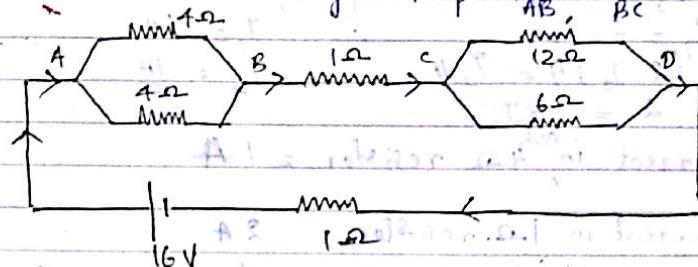- Compute the equivalent resistance of the network
- Obtain the current in each resistor.
- Obtain the voltage drop  $V_{AB}$ ,  $V_{BC}$  and  $V_{CD}$ .



- 4 ohm and 4 ohm are in parallel.

$$\frac{1}{R'} = \frac{1}{4} + \frac{1}{4} = \frac{4+4}{4 \times 4} = \frac{8}{16} = \frac{1}{2}$$

$R' = 2\Omega$   
 12Ω and 6Ω are in parallel.

$$\frac{1}{R''} = \frac{1}{12} + \frac{1}{6}$$

$$\therefore \frac{1+2}{12} = \frac{3}{12}$$

$$\therefore R''' = \frac{12}{3} = 4\Omega$$

∴ Equivalent resistance  $R = R' + R'' + R'''$   
 $= 2 + 1 + 4 = 7\Omega$

(b) Total current  $I = \frac{V}{R_{\text{eq}}}$

$$= \frac{16}{(7+1)}$$

$$= \frac{16}{8} = 2A$$

Consider the resistors between A and B. voltage same.

$$\frac{I_1}{I_2} \times I_1 = \frac{I_2}{I_4} \times I_4$$

$$I_1 + I_2 = 2$$

$$I_1 + I_2 = 2$$

$$I_1 = 2 - I_2$$

$$I_1 = 2 - I_2$$

$$(2 - I_2) + I_2 = 2$$

$$I_2 = 1A$$

$$I_1 = 2 - 1 = 1A$$

$$I_1 = 1A$$

Current in 1Ω resistor = 2A

Current in Consider the resistor between C and D.

$$\frac{I_3}{I_4} \times 12 = \frac{I_4}{I_2} \times 6$$

$$2I_3 = I_4 + 1 = 1$$

$$\frac{I_3}{3} + \frac{I_4}{4} = 2$$

$$2I_3 = 2 - I_3 \Rightarrow 3I_3 = 2$$

$$3I_3 = 2$$

$$I_3 = \frac{2}{3} A$$

$$\therefore I_4 = \frac{4}{3} A$$

Current in 12Ω =  $\frac{2}{3} A$  and 6Ω  
 Current in 6Ω =  $\frac{4}{3} A$

(c)  $V_{AB} = 4 \times 1 = 4V$  Because both are 1Ω resistors

$$V_{BC} = 1 \times 2 = 2V$$


$$V_{CD} = 12 \times \frac{2}{3} = 8V$$

$$= 2 \times 4 = 8V$$

Cells in Series and in Parallel.

Cells in Series.

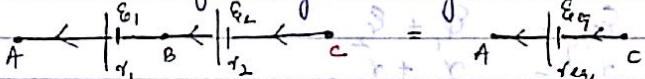Suppose two cells of emfs  $E_1$  and  $E_2$  and internal resistances  $r_1$  and  $r_2$  are connected in series between points A and C. Let I be the current flowing through the series combination.



Let  $V(A)$ ,  $V(B)$ ,  $V(C)$  be the potentials at points A, B and C shown in figure.

The potential difference between the positive and negative terminals of the first cell.

$$V_{AB} = V(A) - V(B)$$

$$\text{by } V_{AB} = \mathcal{E}_1 - I_1 r_1$$

$$V_{BC} = V(B) - V(C)$$

$$\text{by } V_{BC} = \mathcal{E}_2 - I_2 r_2$$

Hence P.d. between the terminals A and C of the combination is

$$V_{AC} = V(A) - V(C)$$

$$= [V(A) - V(B) + V(B) - V(C)]$$

$$= \mathcal{E}_1 - I_1 r_1 + \mathcal{E}_2 - I_2 r_2$$

$$= (\mathcal{E}_1 + \mathcal{E}_2) - I(r_1 + r_2) \quad \text{--- (1)}$$

If we wish to replace the combination by a single cell between A and C of emf  $\mathcal{E}_{eq}$  and internal resistance  $r_{eq}$ , then

$$V_{AC} = \mathcal{E}_{eq} - I r_{eq} \quad \text{--- (2)}$$

Comparing the eqns (1) and (2), we get

$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$$

$$\text{and } r_{eq} = r_1 + r_2$$

For a series combination of n cells,

$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2 + \dots + \mathcal{E}_n$$


$$r_{eq} = r_1 + r_2 + \dots + r_n$$

- (1) the equivalent emf of a series combination of n cells is the sum of their individual emfs.
- (2) The equivalent internal resistance of a series combination of n cells is the sum of their internal resistances.
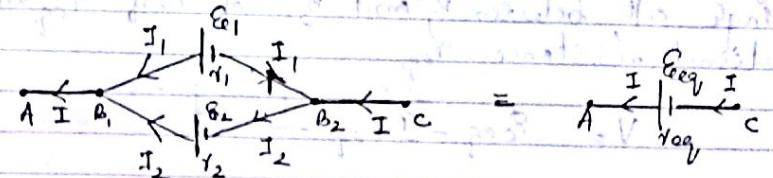
### Cells in Parallel.

Suppose two cells of emfs  $\mathcal{E}_1$  and  $\mathcal{E}_2$  and internal resistances  $r_1$  and  $r_2$  are connected in parallel between two points. Suppose the currents  $I_1$  and  $I_2$  flow from the positive terminals of the two cells towards the junction B and current  $I$  flows out.

$$\text{Thus } I = I_1 + I_2 \quad \text{--- (1)}$$



Let  $V(B_1)$  and  $V(B_2)$  be the potentials at  $B_1$  and  $B_2$ . Then P.d. across the terminals of the first cell.

$$V = V(B_1) - V(B_2) \quad \therefore I_1 = \frac{\mathcal{E}_1 - V}{r_1} \quad \text{--- (2)}$$

P.d. across the terminals of the second cell

$$V = V(B_1) - V(B_2) + \mathcal{E}_2 - I_2 r_2 \quad \therefore I_2 = \frac{\mathcal{E}_2 - V}{r_2} \quad \text{--- (3)}$$

∴ eqn (1) becomes

$$I = \frac{\mathcal{E}_1 - V}{r_1} + \frac{\mathcal{E}_2 - V}{r_2}$$

$$I = \left( \frac{E_1}{r_1} + \frac{E_2}{r_2} \right) - V \left[ \frac{1}{r_1} + \frac{1}{r_2} \right] \quad (4)$$

If we want to replace the combination by a single cell between  $B_1$  and  $B_2$  of emf  $E_{\text{eqn}}$  and internal resistance  $r_{\text{eqn}}$

$$V = E_{\text{eqn}} - I r_{\text{eqn}} \quad (5)$$

$$I r_{\text{eqn}} = E_{\text{eqn}} - V$$

$$I = \frac{E_{\text{eqn}} - V}{r_{\text{eqn}}} \quad (6)$$

$$I = \frac{E_{\text{eqn}} - V}{r_{\text{eqn}}} \quad (7)$$

$$= \frac{E_{\text{eqn}}}{r_{\text{eqn}}} - V \left[ \frac{1}{r_{\text{eqn}}} \right] \quad (8)$$

Comparing eqn (4) and (8)

We can express the above results in a simple way

$$\frac{E_{\text{eqn}}}{r_{\text{eqn}}} = \frac{E_1}{r_1} + \frac{E_2}{r_2} - V \left[ \frac{1}{r_1} + \frac{1}{r_2} \right]$$

$$\text{and } \frac{1}{r_{\text{eqn}}} = \frac{1}{r_1} + \frac{1}{r_2}$$

For a parallel combination of  $n$  cells, we have

$$\frac{E_{\text{eqn}}}{r_{\text{eqn}}} = \frac{E_1}{r_1} + \frac{E_2}{r_2} + \dots + \frac{E_n}{r_n}$$

$$\text{and } \frac{1}{r_{\text{eqn}}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$


### Kirchhoff's Rules.

1. Junction rule: - In an electric circuit, the algebraic sum of currents at any junction is zero. Or - the sum of currents entering a junction is equal to the sum of currents leaving that junction.

Applying junction rule to the junction J of fig  
we get,

$$\sum I = 0$$

$$I_1 + I_2 - I_3 - I_4 = 0$$

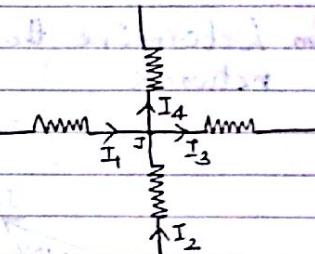

$$I_1 + I_2 = I_3 + I_4$$

Current entering = Current leaving  
the junction

2. Loop rule: - Around any closed loop of a network (Mesh rule), the algebraic sum of changes in potential must be zero. Or, the algebraic sum of the emf's in any loop of a circuit is equal to the sum of the products of

currents and resistances in it.

Mathematically

$$\sum V = 0$$


$$\text{or } \sum E = \sum IR.$$

### Illustration:

Consider the circuit

Applying Kirchhoff's loop rule to the mesh ABCFA

$$E - I_2 R_2 = I_1 R_1 - I_2 R_2$$

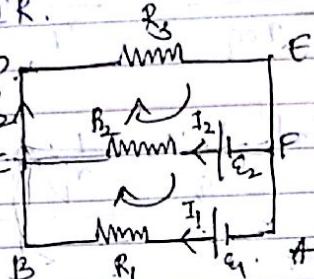


For the mesh CDFFC

$$E_2 = I_2 R_2 + (I_1 + I_2) R_3$$

For the mesh ABDEA

$$E_1 = I_1 R_1 + (I_1 + I_2) R_3$$

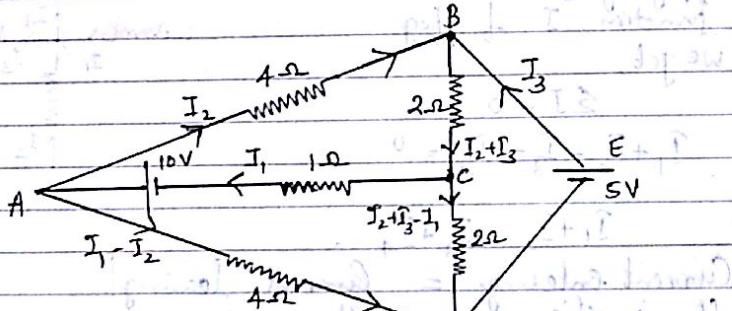Prob. Determine the current in each branch of the network.



For the loop ADCA

$$4(I_1 - I_2) - 2(I_2 + I_3 - I_1) + I_4 = 10$$

$$\Rightarrow 7I_1 - 6I_2 - 2I_3 = 10 \quad \text{--- (1)}$$

To solve (1) to make it of linear form

For the mesh ABCA

$$4I_2 + 2(I_2 + I_3) + I_1 = 10$$

$$\Rightarrow I_1 + 6I_2 + 2I_3 = 10 \quad \text{--- (2)}$$

For the mesh BCDEB

$$2(I_2 + I_3) + 2(I_2 + I_3 - I_1) = 5$$

$$\Rightarrow 2I_1 - 4I_2 - 4I_3 = 5 \quad \text{--- (3)}$$

$$\text{On solving } I_1 = 2.5 \text{ A}, I_2 = \frac{5}{8} \text{ A} \text{ and } I_3 = \frac{15}{8} \text{ A}$$

The currents in the various branches

$$AB = \frac{5}{8} \text{ A} \quad CA = \frac{5}{2} \text{ A} \quad DEB = \frac{15}{8} \text{ A}$$


$$AD = \frac{15}{8} \text{ A}$$

$$CD = 0 \text{ A} \quad BC = \frac{5}{2} \text{ A}$$
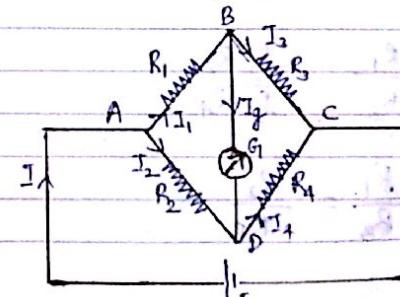
### Wheatstone Bridge

It is an arrangement of four resistances used to determine one of these resistances quickly and accurately in terms of the remaining three resistances.

A Wheatstone bridge consists of four resistances  $R_1, R_2, R_3$  and  $R_4$  connected to form the arms of a quadrilateral ABCD. The battery of emf  $E$  is connected between points A and C and a sensitive galvanometer between B and D as shown in figure.



The resistances are so adjusted that no current flows through the galvanometer. The bridge is then said to be balanced. To the balanced condition:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Proof.

In accordance with Kirchhoff's first law, the currents through various branches are shown. Applying Kirchhoff's II law to the loop ABPA, we get

$$I_1 R_1 + I_2 G - I_2 R_2 = 0$$

For the loop BCDB

$$I_3 R_3 - I_4 G - I_4 R_4 = 0$$

In the balanced condition of the bridge

$$I_g = 0, I_1 = I_3, I_2 = I_4$$

As above eqn becomes

$$I_1 R_1 - I_2 R_2 = 0$$

$$\therefore I_1 R_1 = I_2 R_2$$

$$\therefore I_1 R_1 = I_2 R_2 \quad \text{--- (1)}$$

$$I_3 R_3 - I_4 R_4 = 0$$

$$I_3 R_3 = I_4 R_4$$

$$I_1 R_3 = I_2 R_4 \quad \text{--- (2)}$$

$$\therefore \frac{(1)}{(2)} \frac{I_1 R_1}{I_1 R_3} = \frac{I_2 R_2}{I_2 R_4}$$

$$\therefore \frac{R_1}{R_3} = \frac{R_2}{R_4}$$

This proves the condition for the balanced Wheatstone bridge.

Meter Bridge.


It is the simplest practical application of the Wheatstone bridge that is used to measure an unknown resistance.

Principle: Its working is based on the principle of Wheatstone bridge. When the bridge is balanced

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

Construction: It consists of usually 1m long manganin wire of uniform cross-section stretched along a metre scale fixed over a wooden board with its two ends clamped between two thick metallic slips bent at right angles. The metallic slip has two gaps across which resistors can be connected.

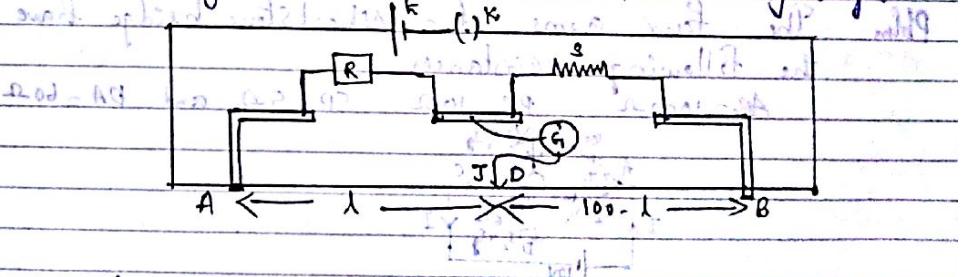The end points where the wire is clamped are connected to a cell through a key. One end of the galvanometer is connected to the metallic slip midway between the two gaps. The other end of the galvanometer is connected to a jockey.



Working: After taking out a suitable resistance  $R$  from the resistance box, the jockey is moved along the wire until there is no deflection in the

galvanometer. This is the balanced condition of the Wheatstone bridge.

Let D be the balance point on the wire distance l cm from the end A. Then the position AD of the wire has a resistance  $R_{cm} \frac{l}{100}$  where  $R_{cm}$  is the resistance of the wire per unit cm. The portion DB of the wire similarly has a resistance  $R_{cm} \frac{(100-l)}{100}$ . Then according to Wheatstone's principle to

$$\frac{R}{S} = \frac{R_{cm} l}{R_{cm} (100-l)}$$

$$\text{but } \frac{R}{S} = \frac{l}{100-l} \text{ (from above relation)} \\ \text{and } \frac{R}{S} = \frac{100-l}{100+l} \text{ (apply this value in the above eqn)} \\ \text{and we get } \frac{R}{S} = \frac{l}{100-l} \text{ (then to find } S)$$


$$S = R \frac{(100-l)}{l}$$

or the unknown resistance  $S = R \frac{(100-l)}{l}$

Knowing l and R unknown resistance S can be determined.

**Prob:** The four arms of a Wheatstone bridge have the following resistances
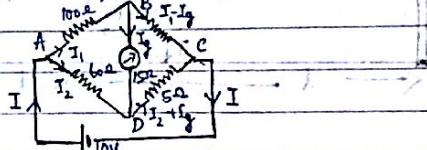
$$AB = 100\Omega, BC = 10\Omega, CD = 5\Omega \text{ and } DA = 60\Omega$$



A galvanometer of  $15\Omega$  resistance is connected across BD. Calculate the current through the galvanometer when p.d. of  $10V$  is maintained across AC.

**Sol:** Considering the mesh BADB, we have

$$100I_1 + 15I_g - 60I_2 = 0$$

$$20I_1 + 3I_g - 12I_2 = 0 \quad \text{--- (1)}$$

for the mesh BCDB, we have

$$10(I_1 - I_g) - 15I_g - 5(I_2 + I_g) = 0$$

$$10I_1 - 30I_g + 5I_2 = 0 \quad \text{--- (2)}$$

$$2I_1 - 6I_g - I_2 = 0 \quad \text{--- (3)}$$

$$\text{For the mesh ADCA, we have}$$

$$100I_2 + 5(I_2 + I_g) = 10 \quad \text{--- (4)}$$

$$65I_2 + 5I_g = 10 \quad \text{--- (5)}$$

$$13I_2 + I_g = 2 \quad \text{--- (6)}$$

$$\text{Xing eqn (2) by } 10I_1 + V = \text{constant}$$

$$20I_1 - 60I_g - 10I_2 = 0 \quad \text{--- (7)}$$

$$20I_1 + 3I_g - 12I_2 = 0 \quad \text{--- (1)}$$

$$(1) - (7) \Rightarrow 63I_g - 2I_2 = 0$$

$$2I_2 = 63I_g \quad \text{--- (8)}$$

$$I_2 = \frac{63}{2} I_g \quad \text{--- (9)}$$

Sub:  $I_2$  in eqn (3)

$$13 \times \frac{63}{2} I_g + I_g = 2 \quad \text{--- (10)}$$

$$I_g \left[ \frac{819}{2} + 1 \right] = 2 \quad \text{--- (11)}$$

$$I_g \left[ \frac{821}{2} \right] = 2 \quad \text{--- (12)}$$

$$I_g = \frac{4}{821} A$$

$$= 0.00487 A$$

$$= 4.87 \times 10^{-3} A$$

$$= 4.87 \text{ mA}$$

### Potentiometer

A potentiometer is a device used to measure an unknown emf or potential difference accurately.

Principle: - The basic principle of a potentiometer is that when a constant current flows through a wire of uniform cross-sectional area and composition, the potential drop across any length of the wire is directly proportional to that length.

$$\text{By Ohm's law } V = IR \\ = I \frac{R}{A} l \quad \text{--- (1)}$$

For a wire of uniform cross-section and uniform composition, resistivity  $\rho$  and area of cross-section  $A$  are constants.


∴ When a steady current  $I$  flows through the wire

$$I \frac{R}{A} = \text{a Constant.}$$

∴ eqn (1) becomes

$$V \propto l.$$

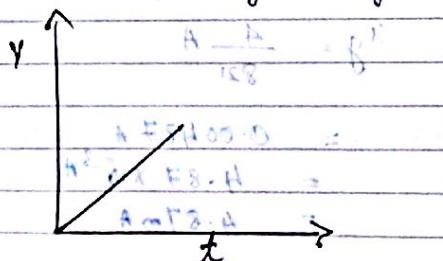This is the principle of a potentiometer. A graph drawn between  $V$  and  $l$  will be a straight line passing through the origin.



### Potential gradient

The potential drop per unit length of the potentiometer wire is known as potential gradient. It is given by

$$K = \frac{V}{l}$$

S.I unit of potential gradient =  $V/m$

Practical unit of potential gradient =  $V/cm$ .

### Applications of a Potentiometer

- Comparison of emfs of two primary cells.

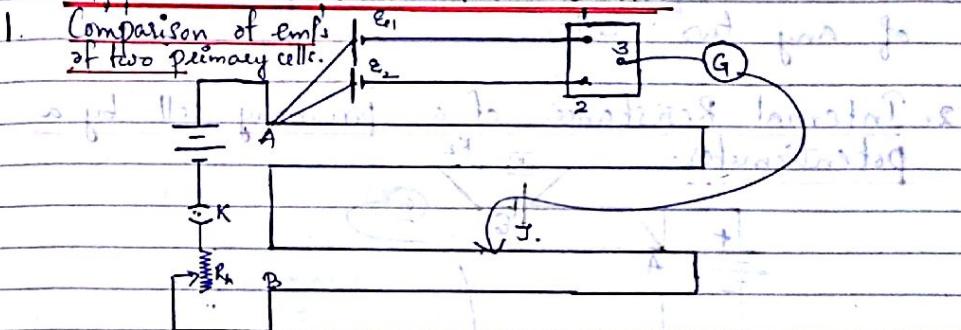


Figure shows the circuit diagram for comparing the emfs of two cells. A constant current is maintained in the potentiometer wire  $AB$  by means of a battery  $B$ . Let  $E_1$  and  $E_2$  be the emfs of the two primary cells which are intended to be compared. The pointer marked 1, 2, 3 forms a two-way key. Consider first position of the key where 1 & 2 are connected so that the galvanometer is connected to the jockey. If the jockey is moved along the wire  $AB$  till the galvanometer shows no deflection. The balancing length is noted from A and is noted as  $l$ . Now  $E_1$  and  $E_2$  are interchanged.

Similarly

By inserting the plug between 2 and 3 so that the galvanometer is connected to  $E_2$ , the balancing length  $l_2$  is obtained for cell  $E_2$ .

Then  $E_2 \propto l_2 \quad \text{--- (2)}$


Hence  $E_1 = k l_1$

$E_2 \propto k l_2$

or  $\frac{E_1}{E_2} = \frac{l_1}{l_2}$

From this eqn we have to compare the emfs of any two cells.
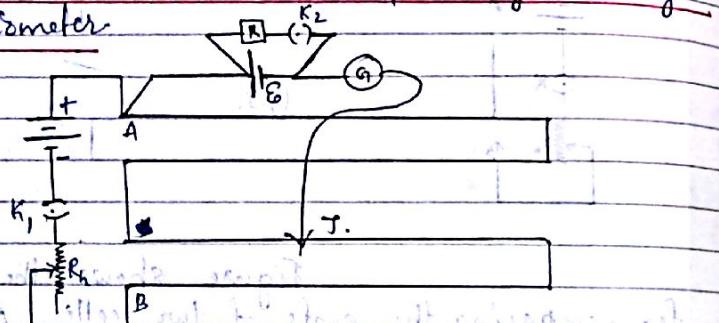
## 2. Internal Resistance of a primary cell by a potentiometer



The positive terminal of the cell of emf  $E$  whose internal resistance is  $r$  is to be measured is connected to the end A of this potentiometer wire and its negative terminal to the galvanometer  $G$  through a jockey  $J$ . A variable resistor  $R$  is connected across this cell through a key  $K_2$ .

When the key  $K_1$  is closed a constant current flows through the potentiometer wire. With key  $K_2$  kept

open move the jockey along  $AB$  till it balances the emf  $E$  of the cell. Let  $l_1$  be the balancing length of the wire then  $E \propto l_1 \quad \text{--- (1)}$

Introduce a resistance  $R$  and close key  $K_2$ . Find the balance point for the terminal potential difference  $V$  of the cell. If  $l_2$  is the balancing length then  $V \propto l_2 \quad \text{--- (2)}$

$$\frac{E}{V} = \frac{l_1}{l_2} \quad \text{or} \quad E = V \frac{l_1}{l_2}$$

But  $E = I(r+R)$  where ' $r$ ' is the internal resistance of the cell. Let  $I$  be the current and  $V = IR$ . A

$$I(r+R) = V \frac{l_1}{l_2}$$

$$\frac{r+R}{R} = \frac{l_1}{l_2} \quad \text{or} \quad r+R = \frac{l_1}{l_2} R$$

$$r = \frac{l_1}{l_2} R - R \quad \text{or} \quad r = R \left( \frac{l_1}{l_2} - 1 \right)$$

From this eqn we can find the internal resistance of a given cell if  $r$  is measured with  $(1)$  and  $r+R$  is measured with  $(2)$ .

Q. Why is potentiometer preferred over galvanometer for measuring the emf of a cell? Ans: In galvanometer there is no provision for

Ans: Potentiometer is a null method device. At null point it does not draw any current from the cell and thus there is no potential drop due to the internal resistance of the cell. It measures the p.d. in an open circuit which is equal to the actual emf of the cell.

On the other hand, a voltmeter draws a small current from the cell for its operation. So it measures the terminal P.D. in a closed circuit which is less than the emf of a cell. That is why a potentiometer is preferred over a voltmeter for measuring the emf of a cell.

### Sensitivity of a Potentiometer:

A potentiometer is sensitive if it is capable of measuring very small potential differences. The sensitivity of a potentiometer depends on the potential gradient along its wire. Smaller the potential gradient greater will be the sensitivity of the potentiometer.

Ques. Why do we prefer a potentiometer with a longer bridge wire?

Ans. A potentiometer with a longer bridge wire has a smaller potential gradient ( $k = \frac{V}{l}$ ). Consequently, it is more sensitive and hence preferred.

Q: How can the sensitivity of potentiometer be increased?

- Ans. Sensitivity can be increased by
- Reducing the potential gradient.
  - Increasing the length of the wire.
  - Reducing the current in the main circuit.

### Additional Numericals [Previous CBSE questions]

Q: When a potentiometer is connected between A & B, the balancing length of the potentiometer wire is 300cm. On connecting the same potentiometer between A and C, the balancing length is 100cm. Calculate the ratio of  $E_1$  and  $E_2$ .



Solu:  $E \propto l$ .

In Case I b/w A and B  $x = ? + ?$

$$E_1 \propto 300 \text{ (constant)}$$

In Case II b/w A and C

$$E_1 - E_2 \propto 100$$

Hence  $\frac{E_1 - E_2}{E_1} = \frac{100}{300}$   $\Rightarrow (3+3) : 3 = (3+3) : 3$


$$1 - \frac{E_2}{E_1} = \frac{3+3}{3} = 3+3$$

$$\frac{E_2}{E_1} = 1 - \frac{1}{3} = \frac{2}{3}$$

$$\therefore \frac{E_1}{E_2} = \frac{3}{2} = 3:2$$

Q: A circuit using a potentiometer and battery of negligible internal resistance is set up as shown to develop a constant potential gradient along the wire AB. Two cells of emfs  $E_1$  and  $E_2$  are connected in series as shown in combinations (1) and (2). The balance points are obtained respectively

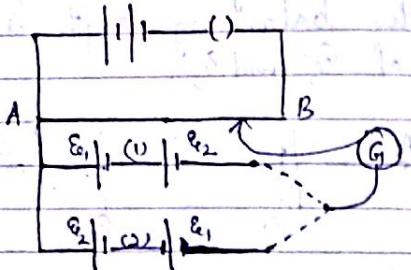at 400 cm and 240 cm from the point A. Find  
 (i)  $\frac{E_1}{E_2}$  (ii) balancing length for the cell  $E_2$  only.



Solu: For the combination (1)

$$E_1 + E_2 \propto 400$$

for the combination (2)

$$E_2 - E_1 \propto 240$$

$$\frac{E_1 + E_2}{E_2 - E_1} = \frac{400}{240} = \frac{5}{3}$$

$$3(E_1 + E_2) = 5(E_2 - E_1)$$

$$3E_1 + 3E_2 = 5E_2 - 5E_1$$

$$3E_1 + 5E_1 = 5E_2 - 3E_2$$

$$8E_1 = 2E_2$$

$$\frac{E_1}{E_2} = \frac{2}{8} = \frac{1}{4} = 1:4$$

(ii)  $E_1 + E_2 \propto 400$

$E_1$  &  $l_1$  are in direct proportion

$$\frac{E_1 + E_2}{E_1} = \frac{400}{l_1} \text{ or } (E_1 + E_2)l_1 = 400E_1$$

$$\frac{E_2}{E_1} = \frac{400}{l_1} \text{ or } l_1 = \frac{400}{E_2/E_1}$$


$$l_1 + 4 = \frac{400}{l_1} \quad \text{but } l_1 = 400 \text{ cm}$$

$$5 = \frac{400}{l_1} + 4 \Rightarrow l_1 = \frac{400}{5} = 80 \text{ cm}$$

$$l_1 = \frac{400}{5} = 80 \text{ cm.}$$

Q. A 10 m long wire of uniform cross-sections of  $20\text{m}^2$  resistance is used as a potentiometer wire. This wire is connected in series with a battery of 5V along with an external resistance of  $480\Omega$ . If an unknown emf  $E_0$  is balanced at 600 cm of this wire. Calculate (i) the potential gradient of the potentiometer

(ii) the value of unknown emf  $E_0$ .

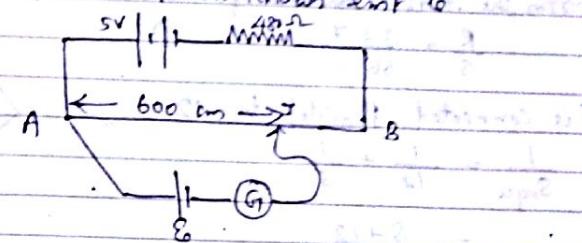

Solu: Current  $I = \frac{V}{R_{AB} + R} = \frac{5}{20 + 480} = \frac{5}{500} = 0.01\text{A}$

$$\text{P.D across the wire } V = IR_{AB} = 0.01 \times 20 = 0.2\text{V}$$

$$\text{Length of the wire } = 10\text{m} = \frac{10}{100} = \frac{1}{10}\text{ km}$$

$$\text{Potential gradient } \times \frac{1}{10} = \frac{0.2}{10} = 0.02\text{V/m}$$

Unknown emf  $E_0$

$$E_0 = k l$$

$$= 0.02 \times 600 \times 10^{-2}$$

$$= 2 \times 10^{-2} \times 600 \times 10^{-2}$$

$$= 1200 \times 10^{-4}$$

$$= \underline{0.12 \text{ V}}$$

Q. In a metre Bridge, the null point is found at a distance of 33.7 cm from A. If now resistance of  $12\Omega$  is connected in parallel with S, the null point occurs at 51.9 cm. Determine the values of R and S.

Ans: From the first balance point

$$\frac{R}{S} = \frac{33.7}{66.3} \quad \text{--- ①}$$

S is connected parallel to  $12\Omega$

$$\frac{1}{S_{\text{equ}}} = \frac{1}{12} + \frac{1}{S}$$

$$= \frac{8+12}{12S}$$

$$\therefore S_{\text{equ}} = \frac{12S}{12+S}$$

and hence the new balance condition

$$\frac{51.9}{48.1} = \frac{R}{S_{\text{equ}}} \quad \text{--- ②}$$


$$\begin{aligned} \frac{51.9}{48.1} &= \frac{R(12+S)}{12S} \\ &= \frac{51.9}{48.1} = \frac{12+S}{12} \times \frac{R}{S} \\ &= \frac{12+S}{12} \times \frac{33.7}{66.3} \end{aligned}$$

$$12+S = \frac{51.9 \times 12 \times 66.3}{48.1 \times 33.7} = \frac{41291.66}{1631.08} = 25.31$$


$$S = 25.31 - 12 = 13.31 \Omega$$

$$\begin{aligned} R &= \frac{33.7 \times 33.7}{66.3} \\ &= \frac{33.7 \times 13.31}{66.3} \\ &= \underline{6.77 \Omega} \end{aligned}$$

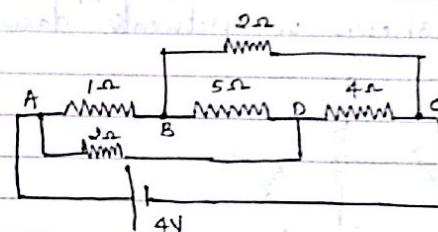Q. Calculate the current drawn from the battery by the network of resistors shown in figure.



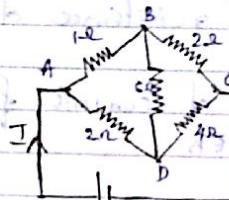Soln: The given network is equivalent to the circuit shown below:



$$\text{Now } \frac{1\Omega}{2\Omega} = \frac{2\Omega}{4\Omega} \quad \left( \frac{R_1}{R_2} = \frac{R_3}{R_4} \right)$$

In the given circuit, the resistance  $5\Omega$  in arm BD is ineffective.

$1\Omega$  and  $2\Omega$  are in series  
 $\therefore R_1 = 1+2 = 3\Omega$

$2\Omega$  and  $4\Omega$  are in series.  
 $R_2 = 2+4 = 6\Omega$


$R_1$  and  $R_2$  are in parallel.

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{6} = \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\therefore R = 2\Omega$$

$$\text{Current } I = \frac{V}{R} = \frac{4}{2} = \underline{\underline{2A}}$$

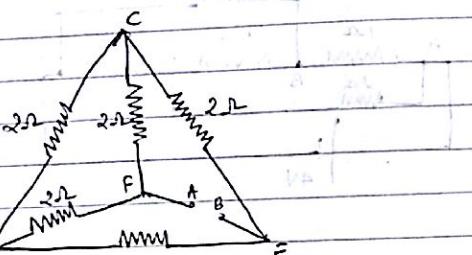Q. A potential difference of  $2V$  is applied between points A and B shown in network drawn in figure.




Calculate

(i) the equivalent resistance of the network between points A and B

(ii) the magnitude of current flowing in the arms AFCFB and AFDEB.

Soln: The equivalent network is shown in

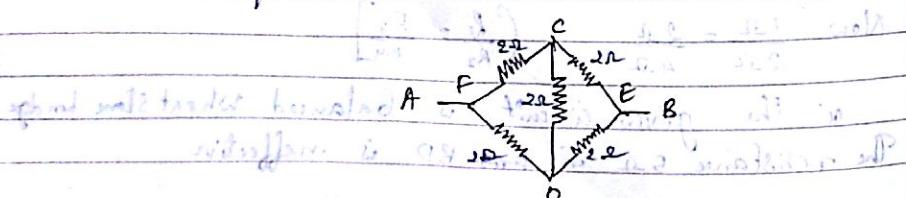

The Bridge is balanced because

$$\frac{2\Omega}{2\Omega} = \frac{2\Omega}{2\Omega}$$

Hence the resistance in arms CD is ineffective.

$$R_1 = 2\Omega + 2\Omega = 4\Omega$$

$$R_2 = 2\Omega + 2\Omega = 4\Omega$$

$$\text{Total resistance } \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$

$$\therefore R = 2\Omega$$


$$\text{Total current } I = \frac{V}{R} = \frac{2V}{2\Omega} = \underline{\underline{1A}}$$

Current through arms AFCFB = Current through arms AFDEB


$$= \frac{1}{2} A$$

$$= \underline{\underline{0.5A}}$$

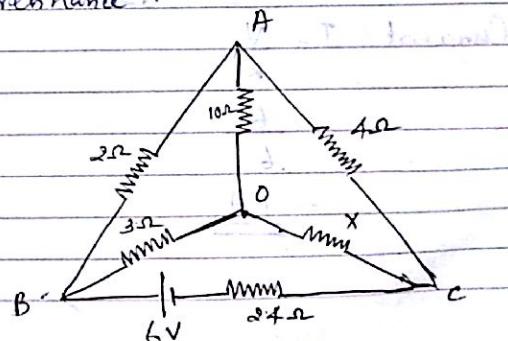Q. Find the value of the unknown resistance  $X$  in the following circuit. If no current flows through the section AO. Also calculate the current drawn by the circuit from the battery of emf  $6V$  and negligible internal resistance.



Solu.

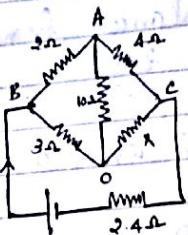

If no current flows through the resistors AO  
 $\therefore$  the bridge is balanced  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$\frac{2}{4} = \frac{3}{x}$$

$$\text{or } x = \frac{4 \times 3}{2} = \underline{\underline{6\Omega}}$$

2Ω and 4Ω are in series

$$R_1 = 2 + 4 = 6\Omega$$

3Ω and 6Ω are in series

$$\text{and so } R_2 = 3 + 6 = 9\Omega$$

Total resistance of the arms

$$\therefore \frac{1}{R'} = \frac{1}{6} + \frac{1}{9}$$

$$= \frac{9+6}{9 \times 6}$$

$$\text{so } R' = \frac{9 \times 6}{9+6} = \frac{54}{15} = 3.6\Omega$$


$$\text{Total resistance } R = 3.6 + 2.4 = 6\Omega$$

$$\text{Current } I = \frac{V}{R}$$

$$= \frac{6}{6}$$

$$= \underline{\underline{1A}}$$

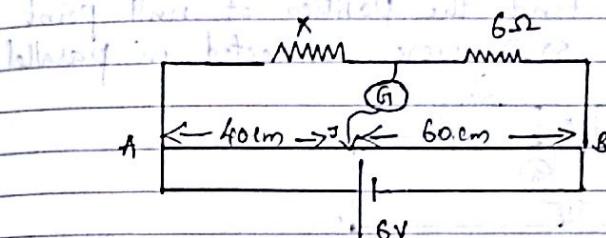Q. In the following circuit a metre bridge is shown in its balanced state. The metre bridge wire has a resistance of  $1\Omega/\text{cm}$ . Calculate the value of the unknown resistance  $x$  and the current drawn from the battery of negligible internal resistance.



Solu.  $l = 40\text{cm}$

$$100 - l = 60\text{cm}$$

$$R = 1\Omega/\text{cm}$$

In balanced condition

$$\frac{x}{6} = \frac{40}{60} \times 1$$

$$\frac{x}{6} = \frac{40}{60}$$

$$x = \frac{40 \times 6}{60} = \underline{\underline{4\Omega}}$$

4Ω and 6Ω are in series

$$\therefore R' = 4 + 6 = 10\Omega$$

Resistance of the wire AB =  $100\Omega$  ( $100 \times 1$ )


These  $R'$  and  $R_{AB}$  are in

$$\frac{1}{R} = \frac{1}{R'} + \frac{1}{R_{AB}} \Rightarrow \frac{1}{10} + \frac{1}{100} = \frac{11}{100}$$

$$R_2 = \frac{100}{11}\Omega$$

$$I = \frac{V}{R} = \frac{6}{\frac{100}{11}} = \frac{66}{100} = \underline{\underline{0.66A}}$$

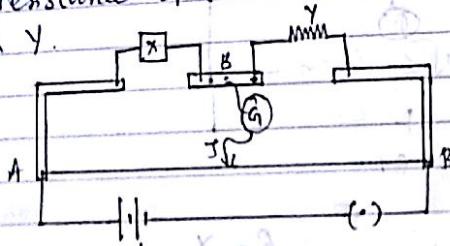Q. The given figure shows the experimental setup of a metre bridge. The null point is found to be 60cm away from the end A with X and Y in positions as shown. When the resistance of  $15\Omega$  is connected in series with Y, the null point is found to shift by 10cm towards the end A of the wire. Find the position of null point if resistance of  $30\Omega$  were connected in parallel with Y.



Soln. In I Case

$$\frac{x}{y} = \frac{60}{40} \quad \text{using formula } \frac{x}{y} = \frac{l}{d}$$

$$\frac{x}{y} = \frac{3}{2} \quad \text{--- (1)}$$

In II Case

$$\frac{x}{y+15} = \frac{50}{50} = 1 \quad \text{--- (2)}$$

$$\frac{(1)}{(2)} \frac{x \times y + 15}{y} = \frac{3}{2}$$

$$\frac{y+15}{y} = \frac{3}{2} \Rightarrow 2y + 30 = 3y \Rightarrow y = 30\Omega$$

$$1 + \frac{15}{y} = \frac{3}{2} \Rightarrow 1 + \frac{15}{30} = \frac{3}{2} \Rightarrow 1 + \frac{1}{2} = \frac{3}{2} \Rightarrow 1 = \frac{3}{2} - \frac{1}{2} = \frac{2}{2} = 1$$

$$\frac{15}{y} = \frac{3}{2} - 1 = \frac{3-2}{2} = \frac{1}{2}$$

$$\therefore y = 30\Omega$$

$$\text{Add } 15 \text{ to both sides} \Rightarrow \frac{15+15}{y} = \frac{3+15}{2} = \frac{18}{2} = 9 \Omega$$

$$\frac{x}{y} = \frac{3}{2} \rightarrow \text{and then multiply both sides by } y$$

$$x = \frac{3 \times 30}{2} = \underline{\underline{45\Omega}}$$

When a resistance of  $30\Omega$  is connected in parallel with Y

$\therefore$  the equivalent resistance

$$\frac{1}{Y'} = \frac{1}{30} + \frac{1}{30} = \frac{2}{30} = \frac{1}{15}$$

$$= \frac{Y+30}{30}$$

and a equivalent branch is  $\frac{Y+30}{30}$  from A to B  
which has length  $l$ .  $\therefore Y' = \frac{30Y}{Y+30}$  which is  $\frac{30}{40}$

$$\frac{X}{30Y} = \frac{l}{100-1}$$

$$\frac{15}{\frac{900}{40}} = \frac{l}{100-1}$$

$$\frac{15 \times 60}{900} = \frac{l}{100-1}$$

$\therefore$   $l = 3(100-1) = l = 300 \text{ cm from A to B}$

$\therefore$   $l = 300 - 30l \Rightarrow 300 = 30l \Rightarrow l = 10\text{ cm}$

$\therefore$   $l = 300 - 30 \times 10 = 0 \text{ cm}$

$\therefore$   $l = \frac{300}{4} = 75\text{ cm}$

Q. In a discharge tube the no. of hydrogen ions (protons) drifting across a cross-section per second is  $1 \times 10^{18}$  while the number of electrons drifting in the opposite direction across another cross-section is  $2.7 \times 10^{18}$  per second. If the Supply Voltage is  $230V$ , what is

the effective resistance of the tube?

$$\text{Sol. } I = ne$$

$$= 2(n_e + n_p)e$$

$$= (2.7 \times 10^{18} + 1 \times 10^8) \times 1.6 \times 10^{-19}$$

$$= 3.7 \times 10^{18} \times 1.6 \times 10^{-19}$$

$$R = \frac{V}{I} = \frac{280}{0.592} = 488.5 \Omega$$

Ques A current of  $2\text{mA}$  is passed through a colour coded carbon resistor with first, second and third rings of yellow, green and orange colours. What is the voltage drop across the resistor?

$$\text{Sol. } R = 45 \times 10^3 \Omega$$

$$I = 2\text{mA} = 2 \times 10^{-3} \text{A}$$

$$V = RI$$

$$= 45 \times 10^3 \times 2 \times 10^{-3}$$

$$= 90 \text{V}$$

Q. A wire of  $10\Omega$  resistance is stretched to thrice its original length. What will be the (i) new resistivity and (ii) new resistance?

Ans. (i) Resistivity  $\sigma$  remains unchanged because it is the property of the material.

$$(ii) V = Al = A'l' \Rightarrow l' = l/3$$

$$\frac{A'l}{A} = \frac{l}{l'} = \frac{l}{3l} = \frac{1}{3}$$

$$\therefore A' = \frac{A}{3}$$

$$R' = \frac{8l'}{A'}$$

$$= \frac{8 \times 3l}{A/3}$$

$$= 9 \times \frac{8l}{A}$$

$$= 9 \times 10 = 90 \Omega$$

Q. A wire has a resistance of  $16\Omega$ . It is melted and drawn into a wire of half its length. Calculate the resistance of the new wire. What is the percentage change in its resistance?

$$\text{Sol. } V = Al = A'l'$$

$$\text{and } A'l' = \frac{l}{2} = \frac{l}{2l} = 2$$

$$A'l' = 2A$$

$$R' = \frac{8l'}{A'} = \frac{8 \times l/2}{2A} = \frac{1}{4} \frac{8l}{A}$$

$$= \frac{1}{4} \times 16 = 4 \Omega$$

$$\text{Change in resistance} = \frac{R - R'}{R} \times 100$$

$$= \frac{(16 - 4)}{16} \times 100$$

$$= 75\%$$

Q. A Cu wire has a resistance of  $10\Omega$  and an area of cross-section  $1\text{mm}^2$ . A potential difference of  $10\text{V}$  exists across the wire. Calculate the drift speed of electrons if the number of electrons per cubic metre in Cu is  $8 \times 10^{28}/\text{m}^3$ .

$$\text{Solu: } R = 10 \Omega$$

$$A = \frac{1 \text{ mm}^2}{10^6 \text{ m}^2}$$

$$V = 10 \text{ V} \quad n = 8 \times 10^{28} \text{ e}^-/\text{m}^3$$

$$I = nAVqe$$

$$\frac{V}{R} = nAVqe \cdot \frac{1}{2 \times 10^6} = 0.1 \times P =$$

$$\text{Ans: } V_d = \frac{V}{nAeR} = \frac{10}{8 \times 10^{28} \times 10^6 \times 1.6 \times 10^{-19} \times 10} = 0.078 \times 10^3 \text{ m/s}$$

Q. An aluminium wire of diameter 0.24 cm is connected in series to a Cu wire of diameter 0.08 cm. The wires carry an electric current of 10 A. Find (i) current density in the Al wire (ii) drift velocity of e<sup>-</sup>s in the copper wire. Given  $n = 8.4 \times 10^{28} \text{ m}^{-3}$

$$\text{Solu: } d = 0.24 \text{ cm} \quad A = \pi r^2 \quad I = 10 \text{ A}$$

$$d = 0.12 \text{ cm} = 0.12 \times 10^{-2} \text{ m}$$

$$\text{Area} = \pi r^2$$

$$= 3.14 \times (0.12 \times 10^{-2})^2$$

$$= 4.5 \times 10^{-6} \text{ m}^2$$

$$I = 10 \text{ A}$$


$$(i) j = \frac{I}{A} = \frac{10}{4.5 \times 10^{-6}} = 2.2 \times 10^6 \text{ A/m}^2$$

$$(ii) \text{ Area of Cu-wire: } d = \pi r^2 \quad \text{Ans: } A = \pi \times (0.08 \times 10^{-2})^2 = 2 \times 10^{-6} \text{ m}^2$$

$$I = nAVqe$$

$$V_d = \frac{I}{nAe} = \frac{10}{8.4 \times 10^{28} \times 2 \times 10^6 \times 1.6 \times 10^{-19}} = 3.7 \times 10^4 \text{ m/s.}$$

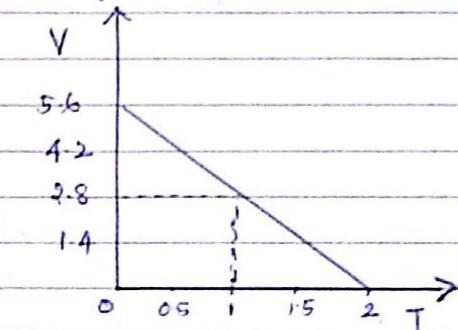Q. 4 cells of identical emf E & internal resistance r are connected in series to a variable resistor. The following graph shows - the variation of terminal voltage of - the combination with the current output:



- (i) What is the emf of each cell used?
- (ii) For what current from the cells, does maximum power dissipation occur in the circuit?
- (iii) Calculate the internal resistance of each cell.

Solu: (i) When  $I = 0$

$$\text{total emf} = \text{terminal p.d}$$

$$4E = 5.6$$

$$E = \frac{5.6}{4} = 1.4 \text{ V}$$

$$(ii) r = \frac{E - V}{I} = \text{Ans: } r =$$

$$\text{TP: } I = 1 \text{ A} \quad V = 2.8 \text{ V}$$

$$\text{i.e. For 4 cell } V = 2.8$$

$$\therefore 4V = 2.8 \quad V = \frac{2.8}{4} = 0.7 \text{ V}$$

$$I = \frac{E - V}{R}$$

$$= 1.4 - 0.7 = 0.7 \Omega$$

(ii) The output power is maximum when internal resistance = external resistance


$$R = 4\Omega$$

$$I_{\text{max}} = \frac{E}{R+1} =$$

Here

$$\begin{aligned} I_{\text{max}} &= \frac{4E}{4\Omega + 1} \\ &= \frac{4E}{2\Omega + 2} = 1.4 \\ &\approx 1A \end{aligned}$$

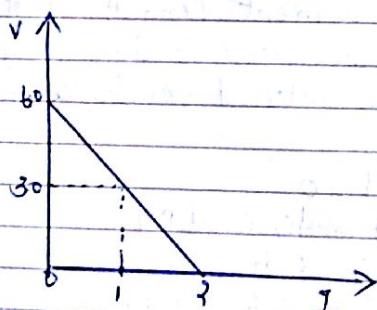Q. The graph shows the variation of terminal potential difference  $V$  across a combination of three cells in series to a resistor versus the current  $I$



(i) Calculate the emf of each cell.

(ii) For what current  $I$  will the power dissipated by the circuit be minimum?

Sol: (i) When  $I = 0$

total emf = terminal pd  
 $3E = 6$

$$E = \frac{6}{3} = 2V$$

(ii) The output power is maximum when internal resistance = external resistance  
 $R = 3\Omega$

$$\begin{aligned} \therefore I_{\text{max}} &= \frac{E}{R+1} \text{ becomes} \\ &= \frac{3E}{3\Omega + 3\Omega} \\ &= \frac{E}{2\Omega} \end{aligned}$$

$$\text{When } I = 1A$$

$$V = 3V$$

as for 3 cells  $V = 3$  Volt

$$\therefore 3V = 3 \text{ Volt}$$

$$V = \frac{3}{3} = 1V$$

$$R = \frac{E-V}{I} = \frac{2-1}{1} = 1\Omega$$

$$\therefore I_{\text{max}} = \frac{2}{2 \times 1}$$

$$= \frac{2}{2} = 1A$$

Q. Two wires of equal length, one of copper and the other of manganin have the same resistance. Which wire be thicker?

Solu: As  $R = \frac{8l}{A}$

$$A = \frac{8l}{R} \quad \text{---(1)}$$

For both wires  $R$  and  $l$  are same  
and  $\rho_{Cu} < \rho_{manganin}$ .

From equ(1)  $A_{Cu} < A_{manganin}$

$\therefore$  manganin wire is thicker than copper wire.

Q: Two wires of equal cross-sectional area, one of copper and other of manganin have the same resistance. Which one will be longer?

Solu:

$$R = \frac{8l}{A}$$

$$l = \frac{RA}{8} \quad \text{---(1)}$$


For both wires  $R$  and  $A$  are same

$$\rho_{Cu} < \rho_{manganin}$$

$\therefore$  from equ(1)  $l_{Cu} > l_{manganin}$

$\therefore$  copper wire is longer than manganin.

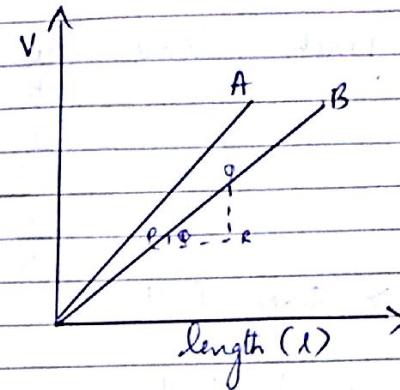Q: The variation of P.D with length in case of two potentiometers A and B is shown. Which of the two is preferred to find E.M.F. of a cell? Give reason for your answer.



Solu:


Slope of the graph  
 $\tan \theta = \frac{CR}{PR}$

$$= \frac{V}{l} = K \text{ (potential gradient)}$$

Slope of line A  $>$  Slope of line B  
 $\therefore K$  of A  $>$  K of B

As the potential gradient increases the sensitivity of potentiometer decreases.  
 $\therefore$  B has less potential gradient  
 $\therefore$  B is preferred over A.

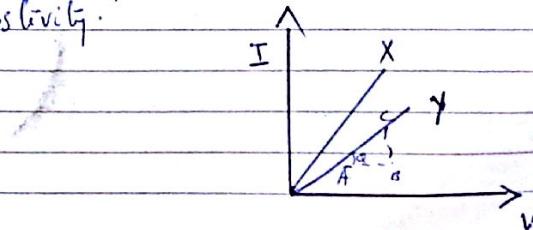Q: The Voltage current variation of two metallic wires X and Y at constant temperature are shown in figure. Assuming that the wires have the same length and the same diameter, explain which of the two wires will have larger resistivity.



Solu: Slope of the graph  $\tan \alpha = \frac{BC}{AB}$

$$= \frac{I}{V}$$
$$= \frac{1}{R}$$

Slope of X > Slope of Y

i.e.  $\frac{1}{R}$  of X >  $\frac{1}{R}$  of Y

or R of X < R of Y.

$\frac{s_{xL}}{A}$  of X <  $\frac{s_{yL}}{A}$  of Y. (length and  
diameter same)

$\therefore s_x < s_y$

Thus wire Y has larger resistivity.